
 


Analog Input and Output

Lecturer: Sri Parameswaran


Notes by: Annie Guo

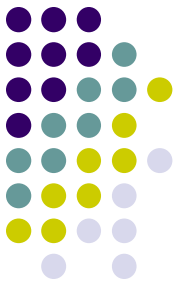




Lecture overview

 - Analog output
 - PMW
 - Digital-to-Analog (D/A) Conversion
- Analog input
 - Analog-to-Digital (A/D) Conversion




PWM Analog Output

- PWM (Pulse Width Modulation) is a way of digitally encoding analog signal levels.
 - Through the use of high-resolution counters, the duty cycle (pulse width/period) of a pulse wave is modulated to encode a specific analog signal level.
- The PWM signal is still digital
 - Its value is either full high or full low.
 - Given a sufficient bandwidth, any analog value can be encoded with PWM.
- PWM is a powerful technique for controlling analog circuits with a processor's digital outputs.
- It is employed in a wide variety of applications
 - E.g. motor speed control

 


PWM Analog Output (cont.)

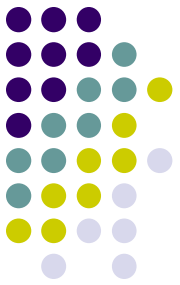- A low-pass filter is required to smooth the input signal and eliminate the inherent noise components in PWM signal.
- The output voltage is directly proportional to the pulse width.
 - By changing the pulse width of the PWM waveform, we can control the output value.



Examples of PWM Signals


Duty cycle=10%

 


Duty cycle=50%



Duty cycle=90%

 

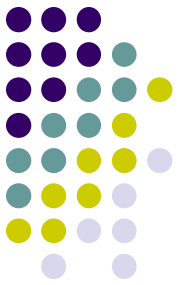



PWM Generation In AVR

- PWM can be obtained through the provided timers.



Recall: Timer0

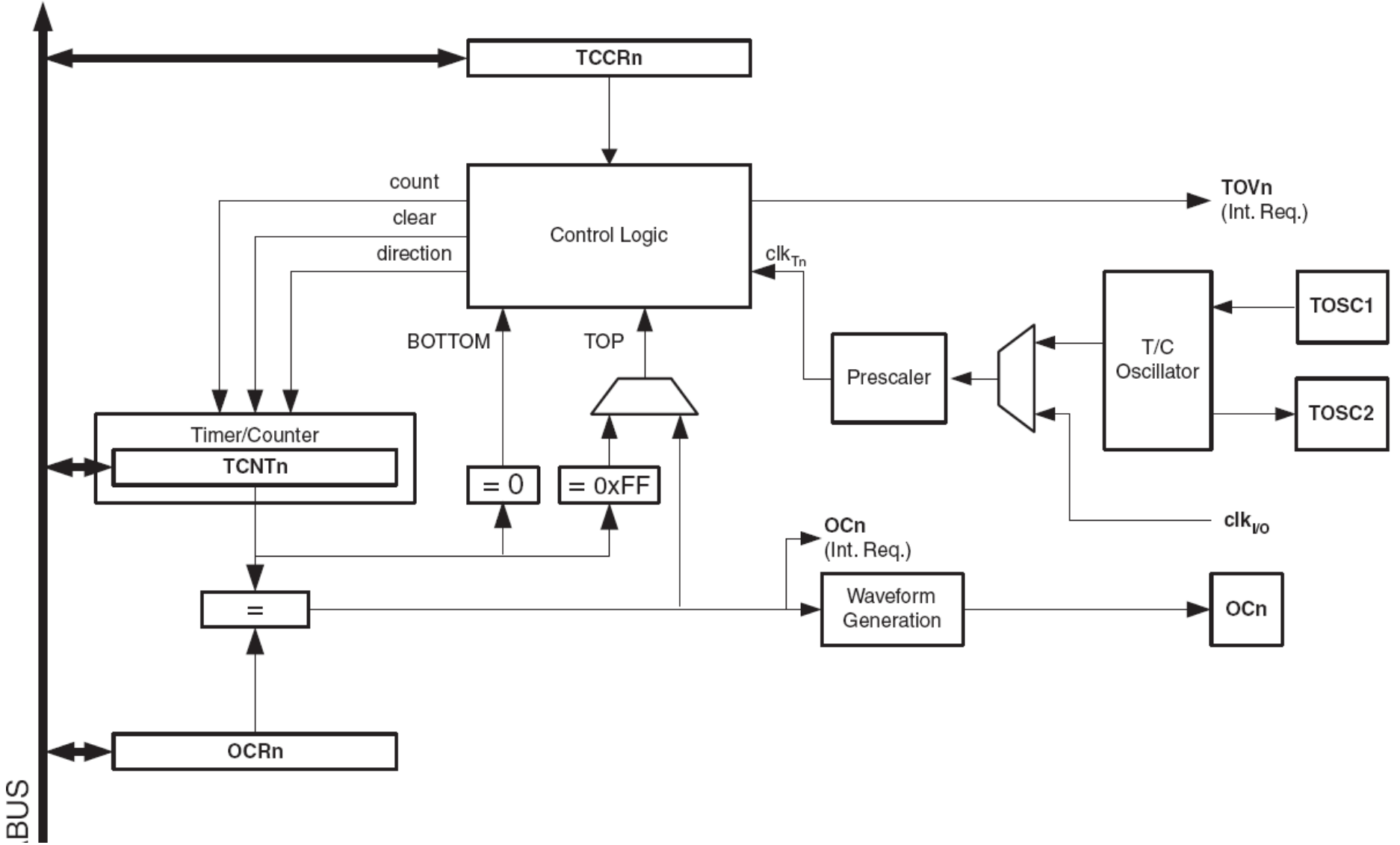

 


Configuration for PWM

- TCCR0A


Bit	7	6	5	4	3	2	1	0	
0x24 (0x44)	TCCR0A								
Read/Write	R/W	R/W	R/W	R/W	R	R	R/W	R/W	
Initial Value	0	0	0	0	0	0	0	0	

Mode	WGM2	WGM1	WGM0	Timer/Counter Mode of Operation	TOP	Update of OCRx at	TOV Flag Set on ⁽¹⁾⁽²⁾
0	0	0	0	Normal	0xFF	Immediate	MAX
1	0	0	1	PWM, Phase Correct	0xFF	TOP	BOTTOM
2	0	1	0	CTC	OCRA	Immediate	MAX
3	0	1	1	Fast PWM	0xFF	TOP	MAX
4	1	0	0	Reserved	–	–	–
5	1	0	1	PWM, Phase Correct	OCRA	TOP	BOTTOM
6	1	1	0	Reserved	–	–	–
7	1	1	1	Fast PWM	OCRA	BOTTOM	TOP



CTC

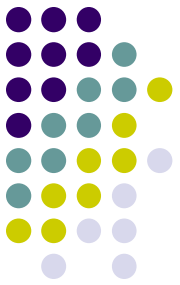



- Clear Timer on Compare Match

 

Fast PWM

  



Phase Correct PWM

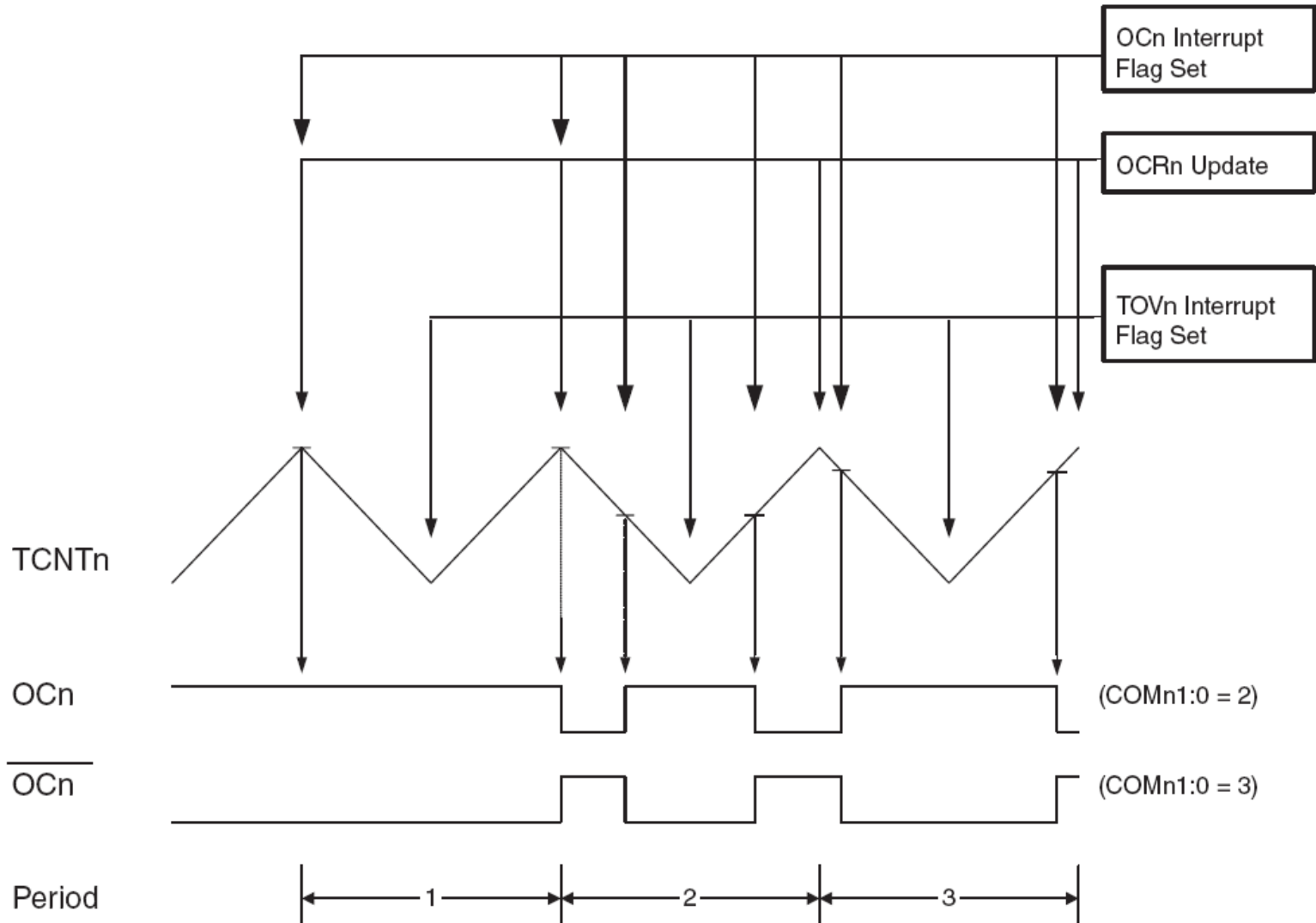 

Example


- Generate a PWM waveform.

 

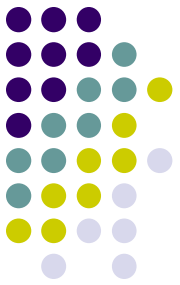

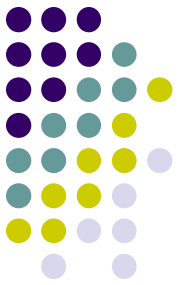Example (solution)

- Use Timer5
 - Set OC5A as output
 - Set the Timer5 operation mode as Phase Correct PWM mode
 - Set the timer clock





Example Code

```
.include "m2560def.inc"
.def temp = r16


    ldi temp, 0b00001000
    sts DDRL, temp           ; Bit 3 will function as OC5A.

    ldi temp, 0x4A         ; the value controls the PWM duty cycle
    sts OCR5AL, temp
    clr temp
    sts OCR5AH, temp
                           ; Set the Timer5 to Phase Correct PWM mode.
    ldi temp, (1 << CS50)
    sts TCCR5B, temp
    ldi temp, (1<< WGM50)|(1<<COM5A1)
    sts TCCR5A, temp
```

Digital-to-Analog Conversion

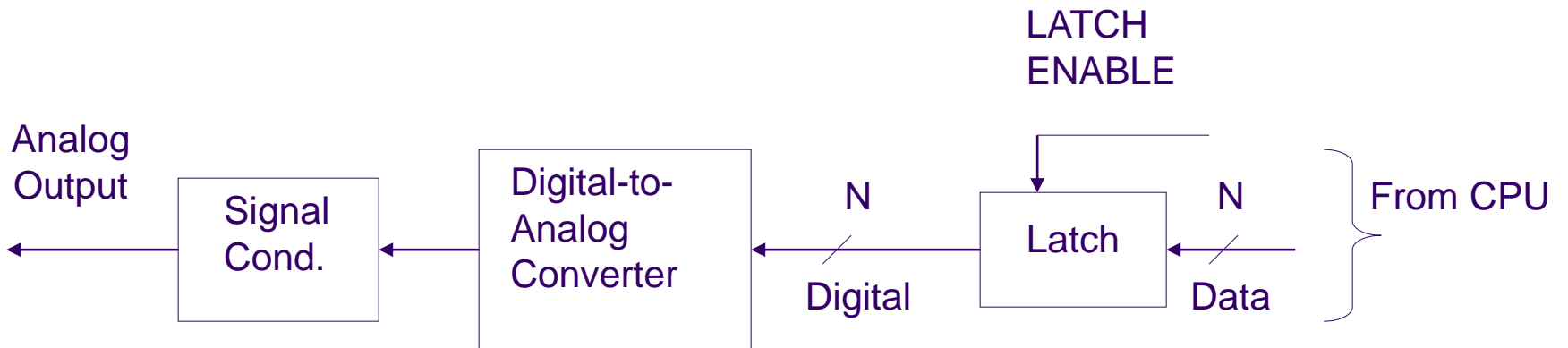
 


Digital-to-Analog Conversion (cont.)

 


- A parallel output interface connects the D/A to the CPU.
- The latches may be part of the D/A converter or the output interface.
- Digital value is converted into continuous value.
- A signal conditioning block may be used as a filter to smooth the quantized nature of the output.
 - The signal conditioning block also provide isolation, buffering and voltage amplification if needed.


Quantized D/A Output

 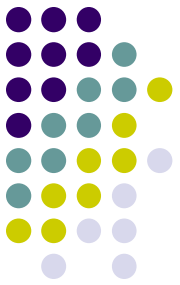


Binary-weighted D/A Converter

 

 
- As the switches for the bits are closed, a weighted current is supplied to the summing junction of the amplifier.
- For high-resolution D/A converters, the binary-weighted type must have a wide range of resistors. This may lead to temperature stability and switching problems.



 

R-2R Ladder D/A Converter

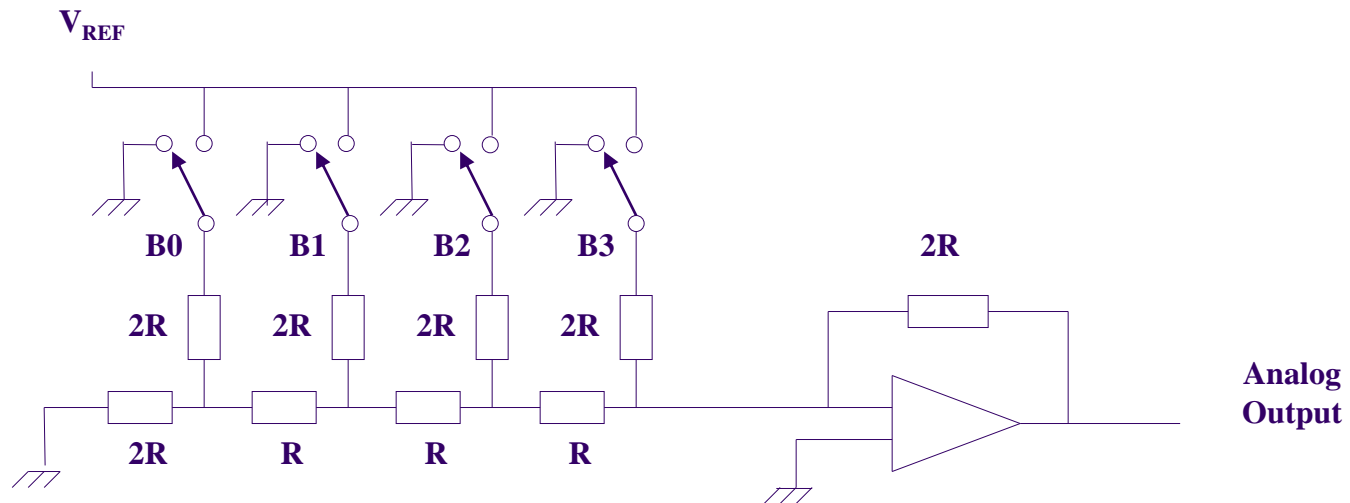- As the switches for the grounded to the reference position, a binary-weighted current is supplied to the summing junction.
- For high-resolution D/A converters, a wide range of resistors are not required.




D/A Converter Specifications





- Resolution and linearity.
 - The resolution is determined by the number of bits and is given as the output voltage corresponding to the smallest digital step, i.e. 1 LSB.
 - The linearity shows how closely the output voltage to the idea values (a straight line drawn through zero and full-scale).
- Settling Time.
 - The time taken for the output voltage to settle to within a specified error band, usually $\pm \frac{1}{2}$ LSB.

D/A Converter Specifications (cont.)


 


- Glitches.
 - A glitch is caused by asymmetrical switching in the D/A switches. If a switch changes from a one to a zero faster than from a zero to a one, a glitch may occur.
 - Consider changing the output code of a 8-bit D/A from 10000000 to 01111111 in the next slide.
 - D/A converter glitch can be eliminated by using a sample-and-hold.



D/A Output Glitch

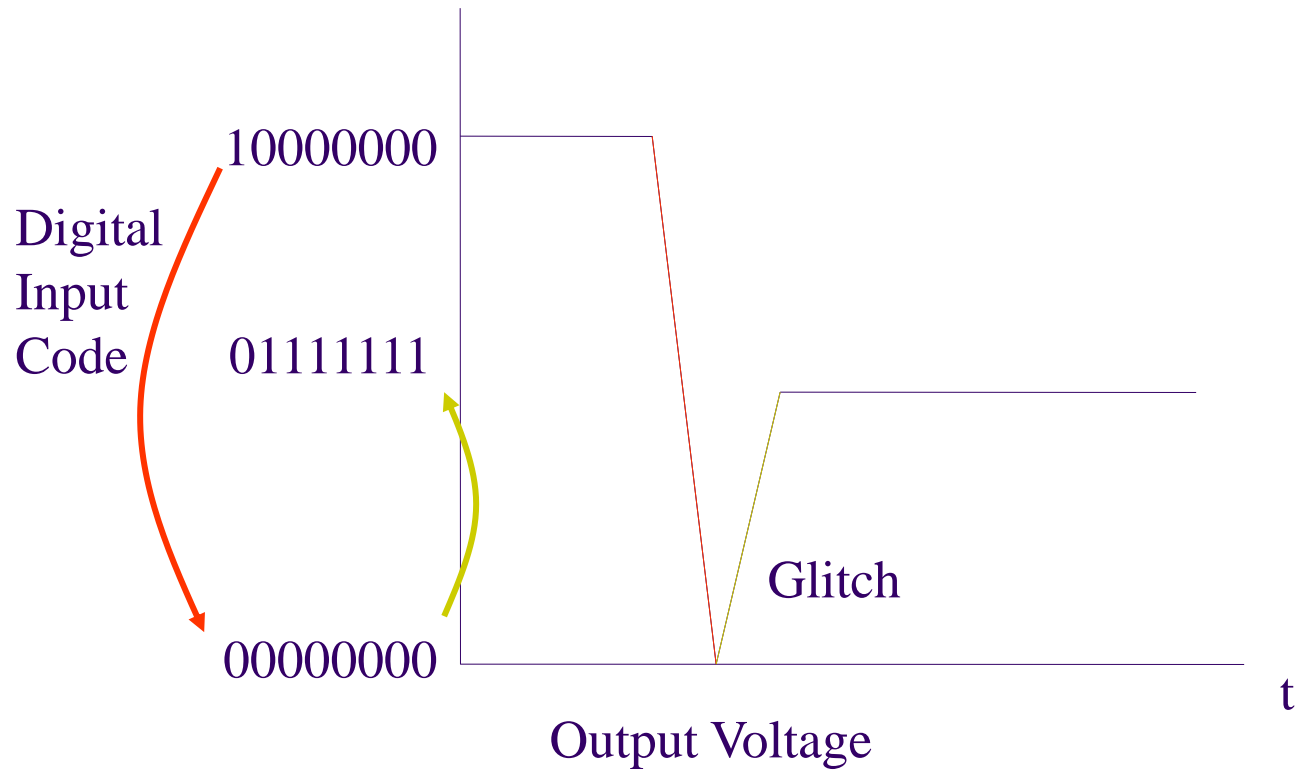 


Deglitched D/A

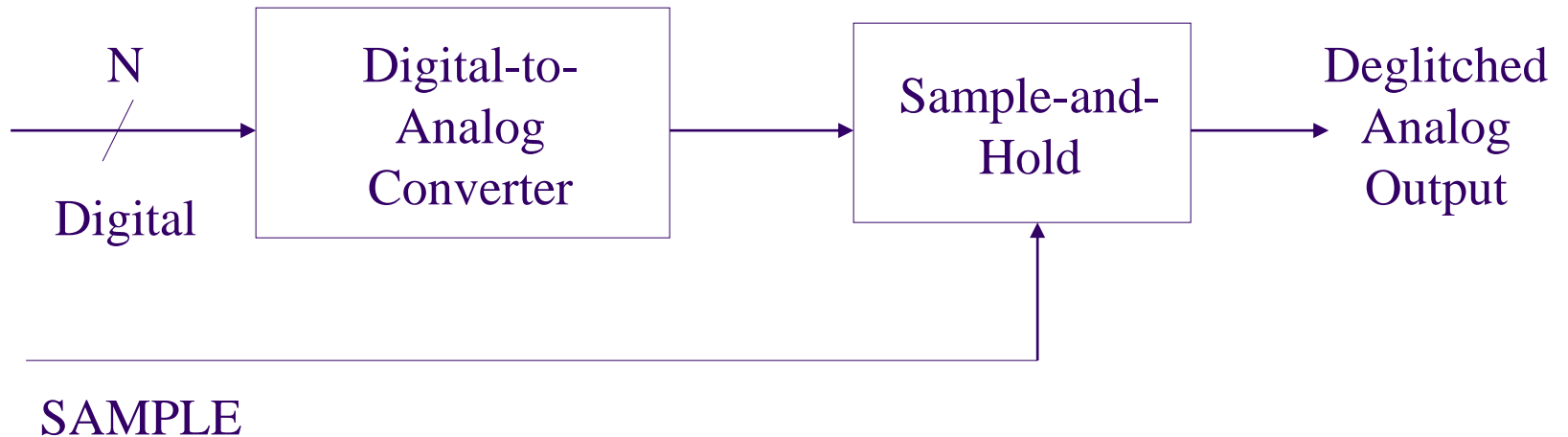 

A/D Conversion

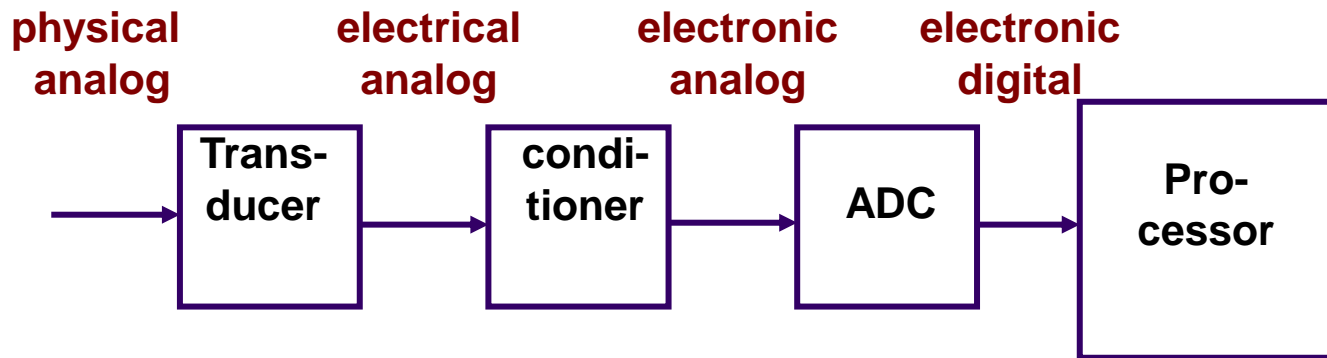 


Data Acquisition and Conversion

 


Procedure of data acquisition and conversion:

- A transducer converts physical values to electrical signals, either voltages or currents.
- Signal conditioner performs the following tasks:
 - Isolation and buffering: The input to the A/D may need to be protected from dangerous voltages such as static charges or reversed polarity voltages.
 - Amplification: Rarely does the transducer produce the voltage or current needed by the A/D. The amplifier is designed so that the full-scale signal from the analog results in a full-scale signal to the A/D.
 - Bandwidth limiting: The signal conditioning provides a low-pass filter to limit the range of frequencies that can be digitized.


Data Acquisition and Conversion (Cont.)

 


- In applications where several analog inputs must be digitized, an analog multiplexer is followed the signal conditioning. It allows multiple analog inputs, each with its own signal conditioning for different transducers.
- The sample-and-hold circuit samples the signal and holds it steady while the A/D converts it.
- The A/D converter converts the sampled signal to digital values.
- The three state gates hold the digital values generated by the A/D converter.

 

Data Acquisition System

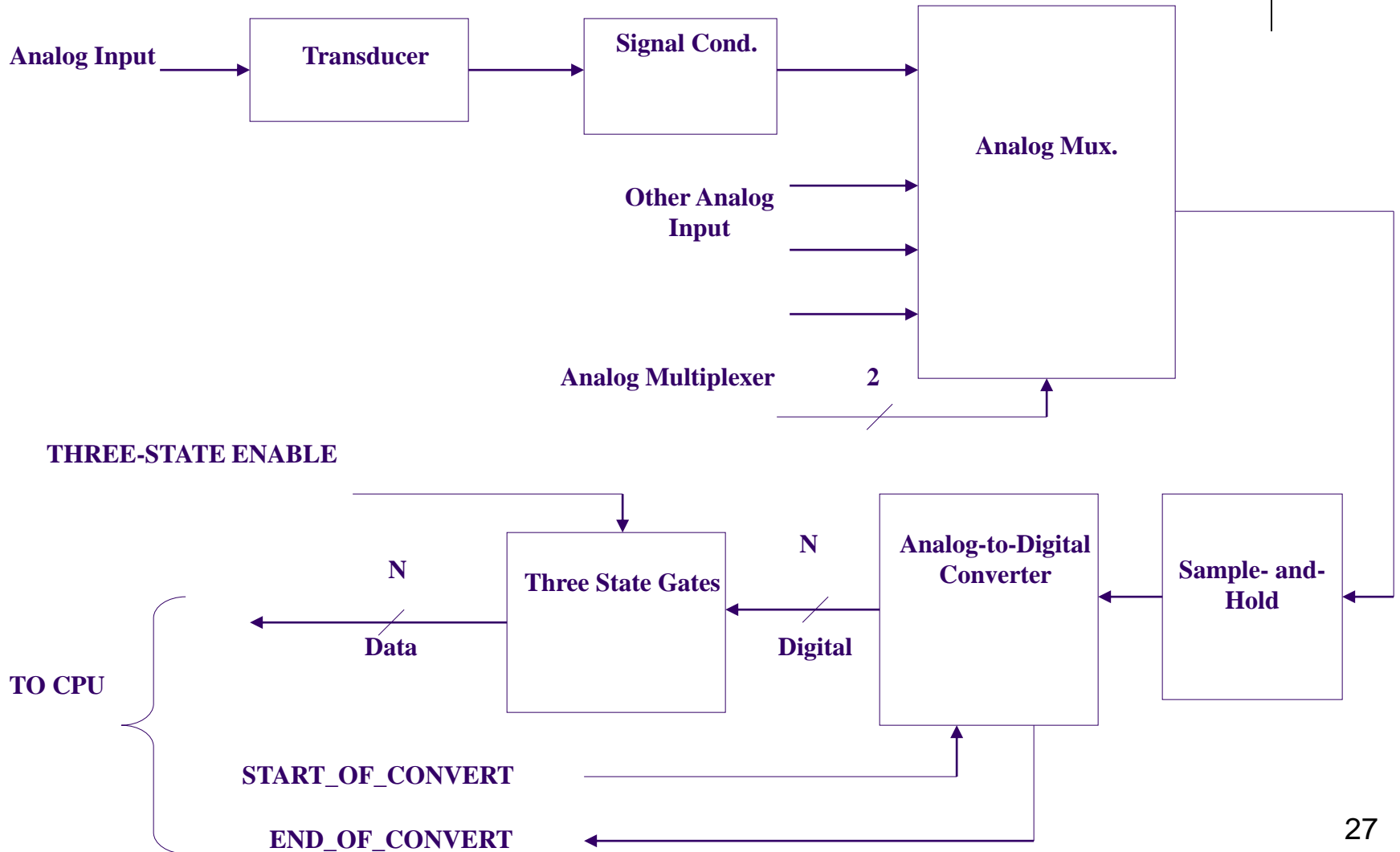


Shannon's Sampling Theorem

 


Claude Shannon's Theorem:

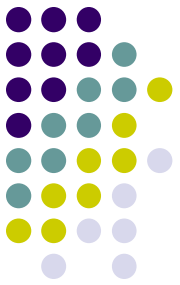
- When a signal, $f(t) = X \sin(2\pi f_{\text{sig}} t)$, is to be sampled (digitized), the minimum sampling frequency must be twice the signal frequency.



Sample Examples

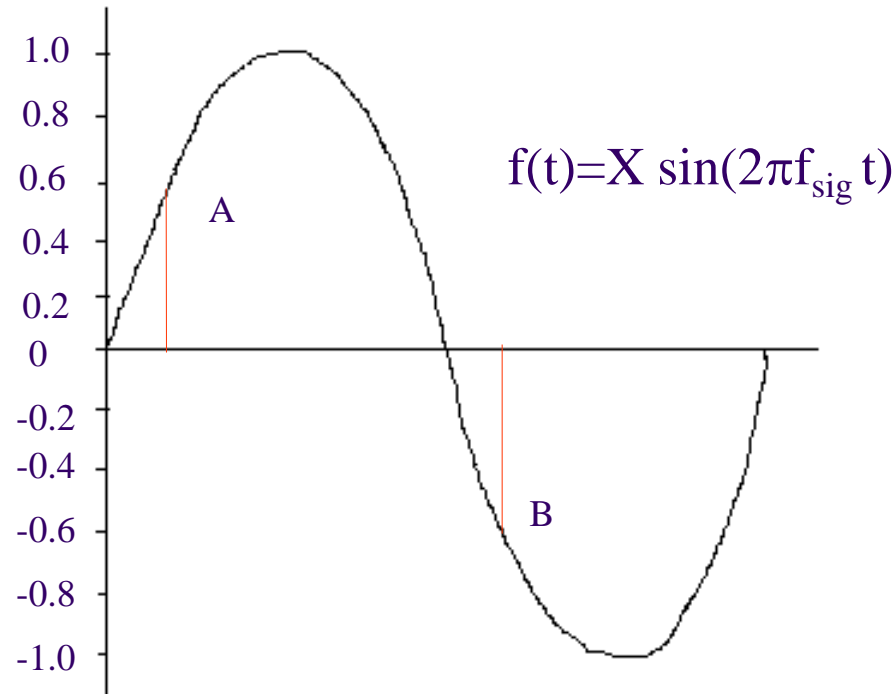
- Sampled at twice of the signal frequency.



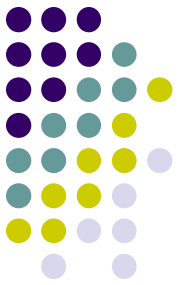


Sample Examples

 - Under-sampled, with sample frequency less than twice of the signal frequency



Shannon's Sampling Theorem and Aliasing

 


- To preserve the full information in the signal, it is necessary to sample at twice the maximum frequency of the signal. This is known as the *Nyquist rate*.
- A signal can be exactly reproduced if it is sampled at a frequency F , where F is greater than or equal to the Nyquist rate.
- If the sampling frequency is less than Nyquist rate, the waveform is said to be under-sampled.



Shannon's Sampling Theorem and Aliasing (Cont.)



 
- Undersampled signal, when converted back into a continuous time signal, will exhibit a phenomenon called *aliasing*.
- Aliasing is the presence of unwanted components in the reconstructed signal. These components were not present when the original signal was sampled.




Successive Approximation Converter

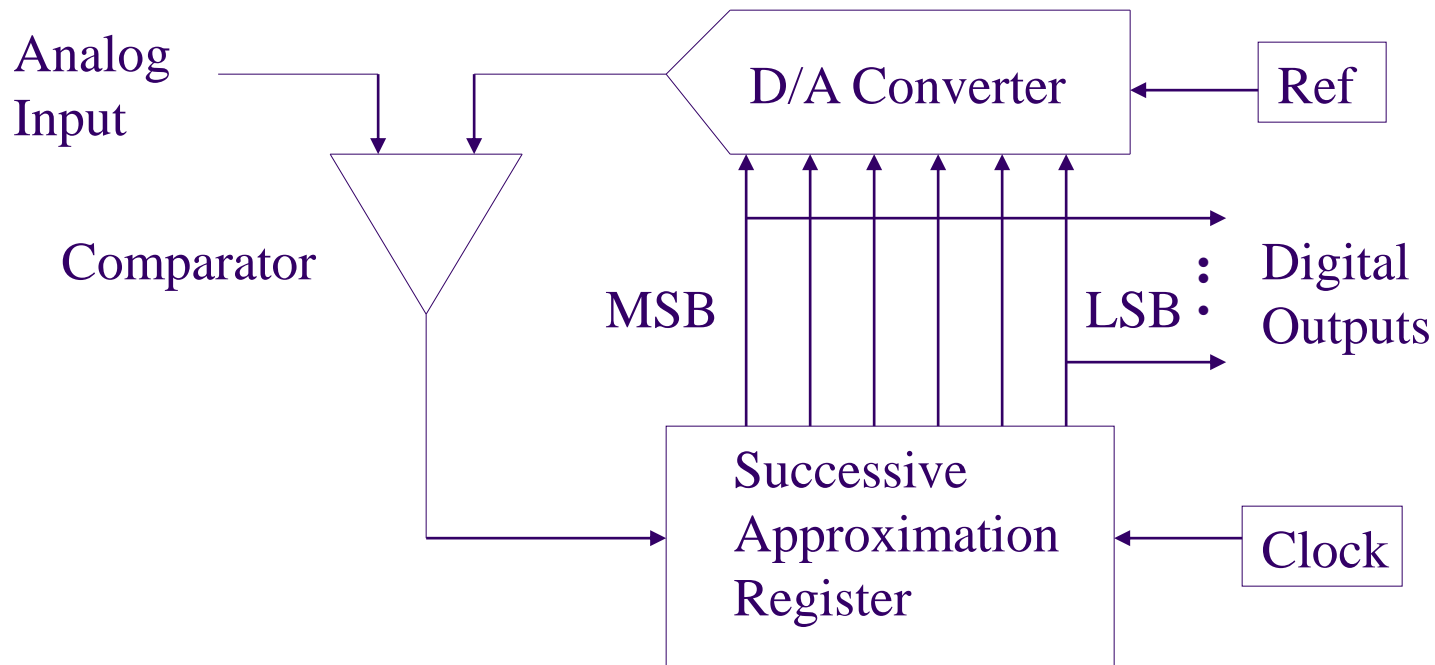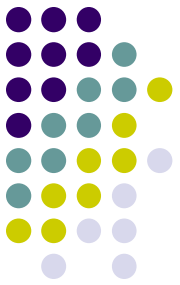


Successive Approximation A/D Converter

 


- Each bit in the successive approximation register is tested, starting at the most significant bit and working toward the least significant bit.
- As each bit is set, the output of the D/A converter is compared with the input.
- If the D/A output is lower than the input signal, the bit remains set and the next bit is tried.
- N times are required to set and test each bit in the successive approximation register.

 


Parallel A/D Converter

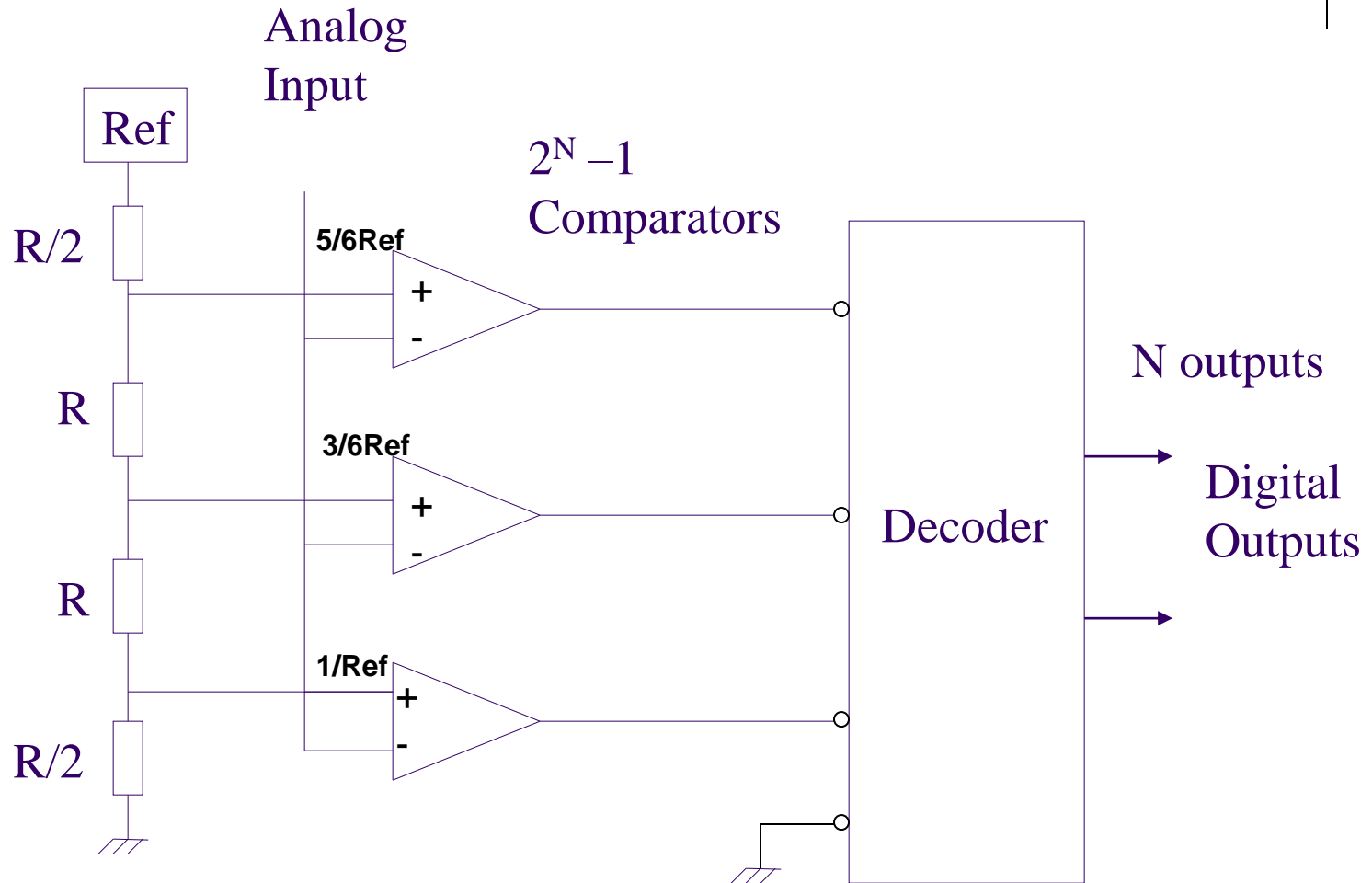

 


Parallel A/D Converter

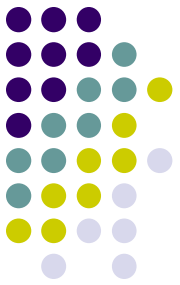
- An array of 2^N-1 comparators and produces an output code in the propagation time of the comparators and the output decoder.
- Fast but more costly in comparison to other designs.
- Also called flash A/D converter.



Two-Stage Parallel A/D Converter

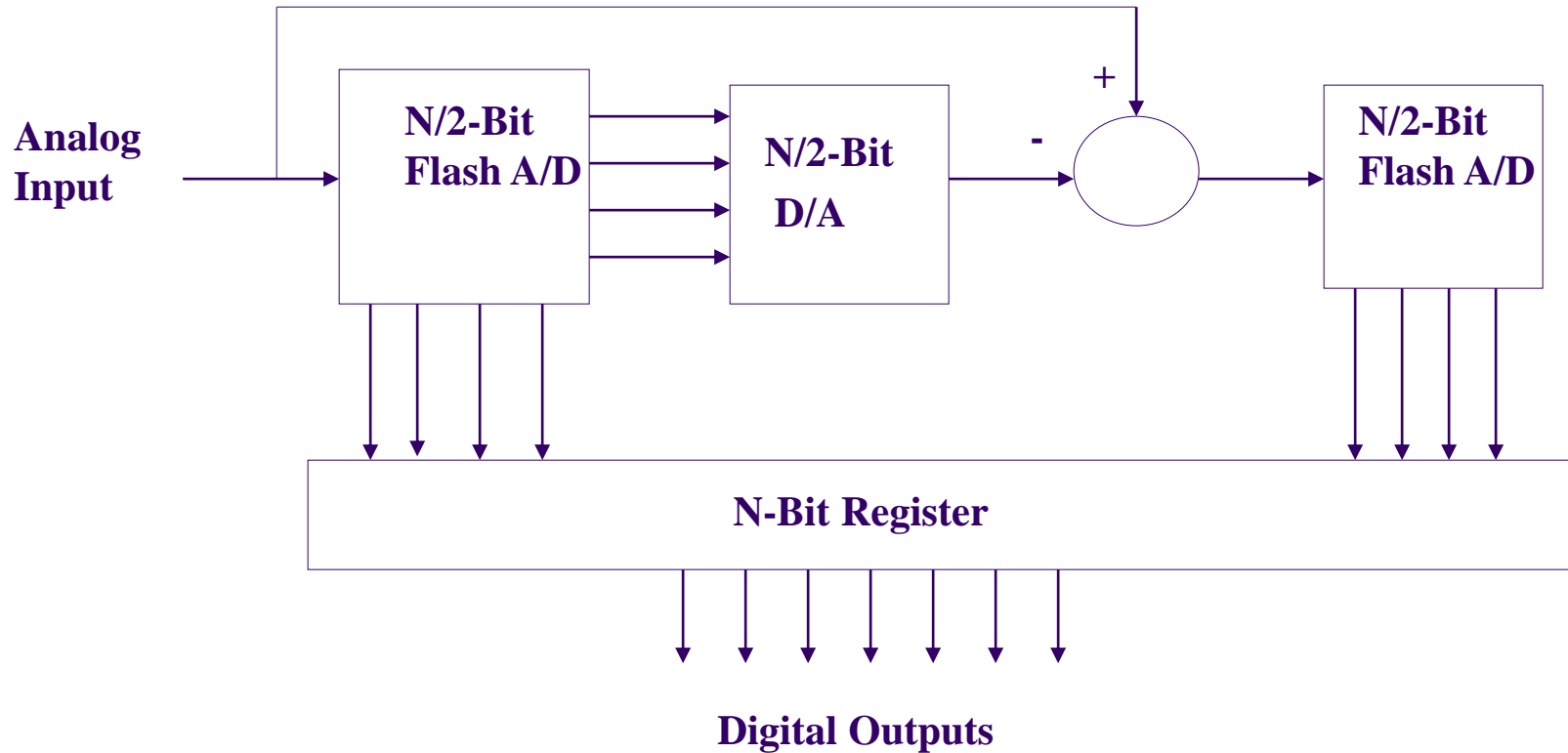


Two-Stage Parallel A/D Converter

 

- The input signal is converted in two pieces.
 - First, a coarse estimate is found by the first parallel A/D converter. This digital value is sent to the D/A and summer, where it is subtracted from original signal.
 - The difference is converted by the second parallel converter and the result combined with the first A/D to give the digitized value.
- It has nearly the performance of the parallel converter but without the complexity of $2^N - 1$ comparators.
- It offers high resolution and high-speed conversion for applications like video signal processing.

A/D Converter Specifications

 

- Conversion time

- The time required to complete a conversion of the input signal.
- Establishes the upper signal frequency limit that can be sampled without aliasing.

$$f_{MAX}=1/(2*\text{conversion time}) \quad (1)$$

- Resolution

- The number of bits in the converter gives the resolution and thus the smallest analog input signal for which the converter will produce a digital code.

- It may be given in terms of the full-scale input signal:

$$\text{Resolution}=\text{full-scale signal}/2^n \quad (2)$$

- It is often given as the number of bits, n ; or stated as one part in 2^n .
- Sometimes it is given as a percent of maximum.

A/D Converter Specifications (Cont.)



- Accuracy


- Relates to the smallest signal (or noise) to the measured signal.
- Given as a percent and describes how close the measurement is to the actual value.

The signal is accurate to within $100\% * V_{\text{RESOLUTION}}/V_{\text{SIGNAL}}$ (3)

- Linearity



- The derivation in output codes from the real value (a straight line drawn through zero and full-scale).
- The best that can be achieved is $\pm 1/2$ of the least significant bit ($\pm 1/2$ LSB).

A/D Converter Specifications (Cont.)

 


- Missing codes.
 - A missing code could be caused by an internal error, especially by the D/A converter in a successive approximation converter.
- Aperture time.
 - The time that the A/D converter is “looking” at the input signal.
 - It is usually equal to the conversion time.


A/D Converter Specifications (Cont.)

  

A/D linearity

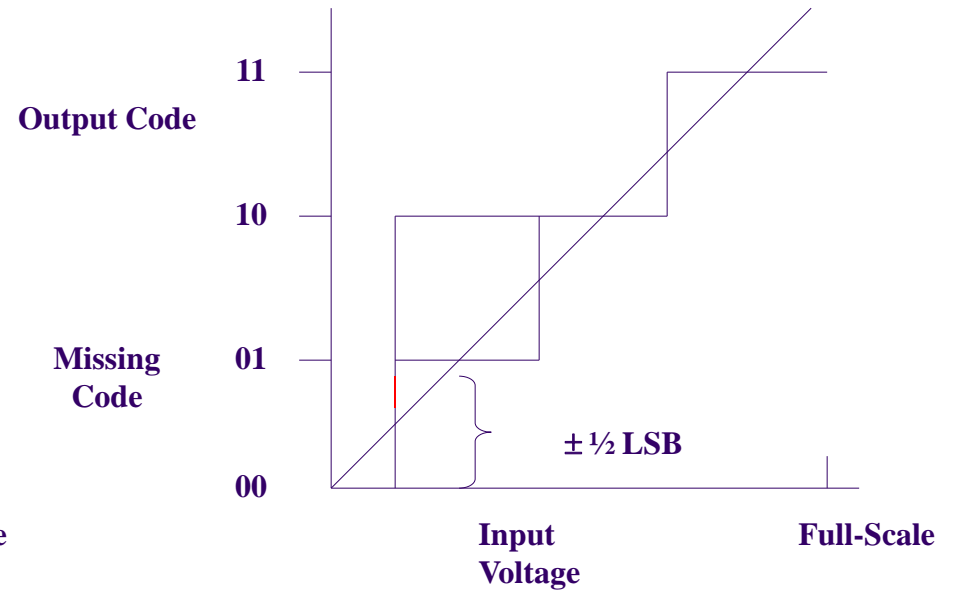


A/D missing codes

 

A/D Errors

- Three sources of errors in A/D conversion:
- Noise:
 - All signals have noise.
 - Need to reduce noise or choose the converter resolution appropriately to control the peak-to-peak noise.
- Aliasing:
 - The errors due to aliasing is difficult to quantify.
 - They depend on the relative amplitude of the signals at frequencies below and above the Nyquist frequency.
 - The system design should include a low-pass filter to attenuate frequencies above the Nyquist frequency.

 



A/D Errors (cont.)

- Aperture.
 - A significant error in a digitizing system is due to signal variation during the aperture time.
 - A good design will attempt to have the uncertainty, ΔV , be less than one least significant bit.
 - A design equation for the aperture time, t_{AP} , in terms of the maximum signal frequency, f_{MAX} , and the number of bits in the A/D converter is


$$t_{AP} = 1 / (2 \pi f_{MAX} 2^n) \quad (4)$$

- The aperture time needed to reduce the error to is surprisingly short.

A/D Errors (Cont.)

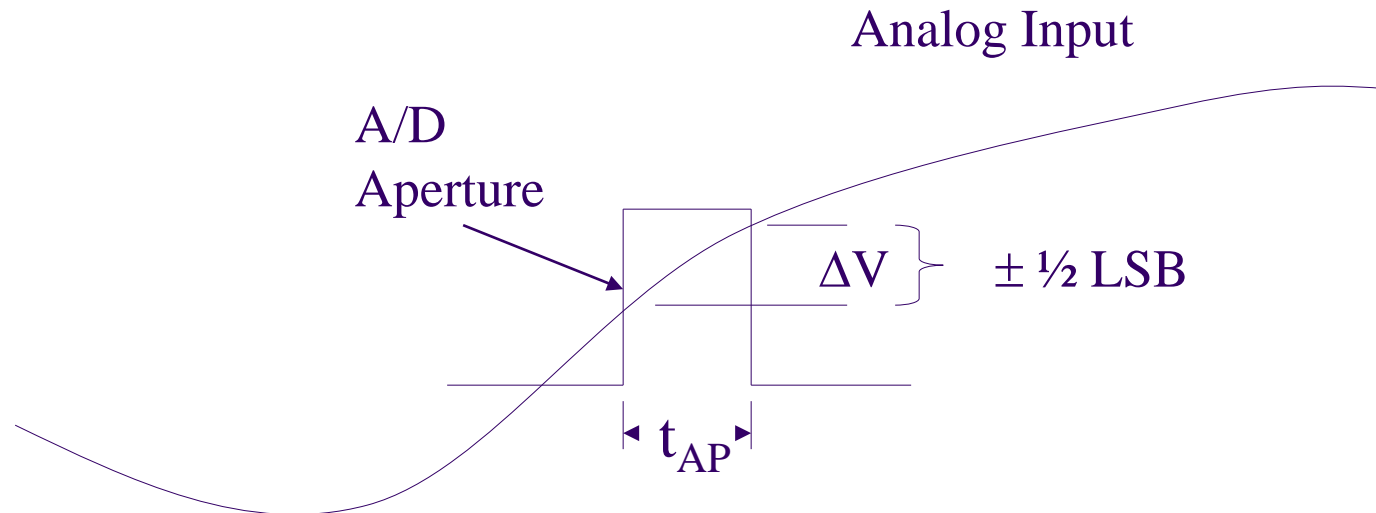 

Aperture time error

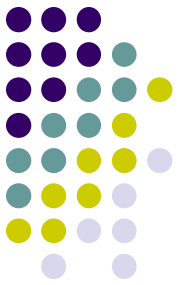

Reading Material

- Chapter 11: Analog Input and Output. Microcontrollers and Microcomputers by Fredrick M. Cady.
- Timers/Counters. AVR Mega2560 Data Sheet.
 - PWM



Homework


1. With the AVR lab board, connect PB7 to a LED and run the following code. What did you observe?

```
.include "m2560def.inc"
.def temp=r16

ldi temp, 0b00001000
sts DDRL, temp ; Bit 3 will function as OC5A.

ldi temp, 0x4A ; the value controls the PWM duty cycle
sts OCR5AL, temp
clr temp
sts OCR5AH, temp


; Set the Timer5 to Phase Correct PWM mode.
ldi temp, (1 << CS50)
sts TCCR5B, temp
ldi temp, (1<< WGM50)|(1<<COM5A1)
sts TCCR5A, temp
```

 

Homework

2. The A/D converter conversion time is 100 μ s. What is the maximum frequency that can be digitalized without aliasing occurring?

Homework

 

3. A transducer is to be used to find the temperature over a range of -100 to 100°C . We are required to read and display the temperature to a resolution of $\pm 1^{\circ}\text{C}$. The transducer produces a voltage from -5 to $+5$ volts over this temperature range with 5 millivolts of noise. Specify the number of bits in the A/D converter (a) based on the dynamic range and (b) based on the required resolution.